

1

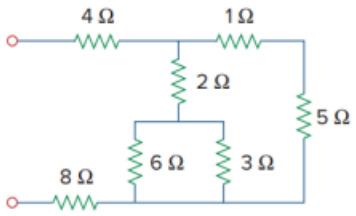Find R_{eq} for the circuit shown in Fig.




2

Determine the value of voltage

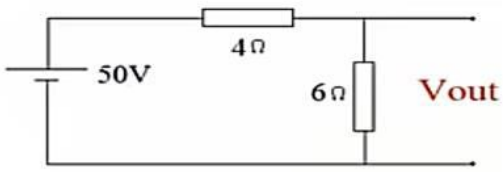


3





Determine the values of i_1, and i_2

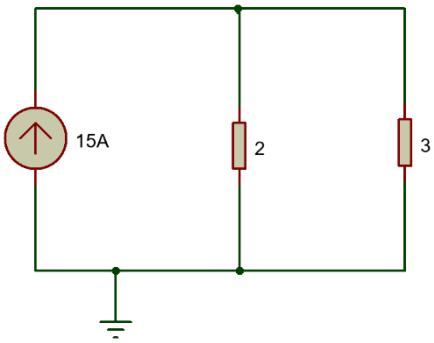

4

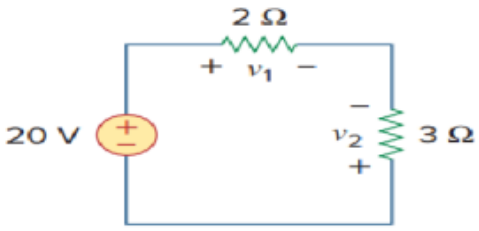
For the circuit in Fig. (a), find voltages v_1 and v_2.



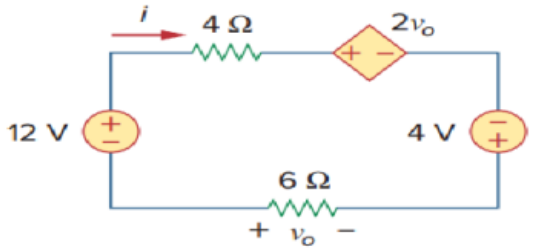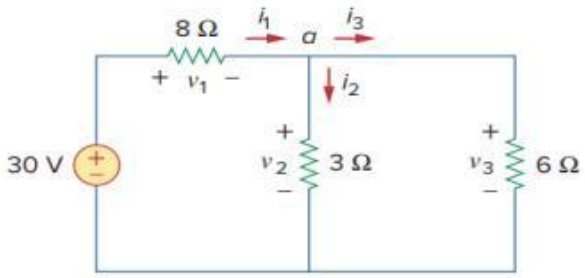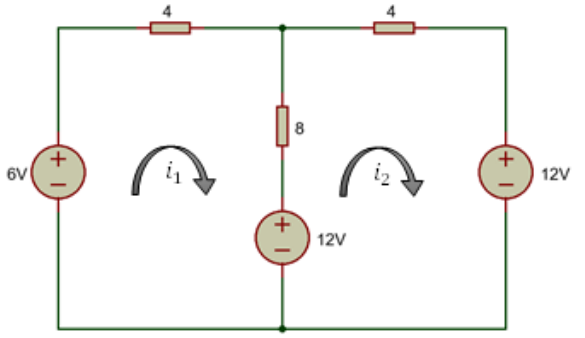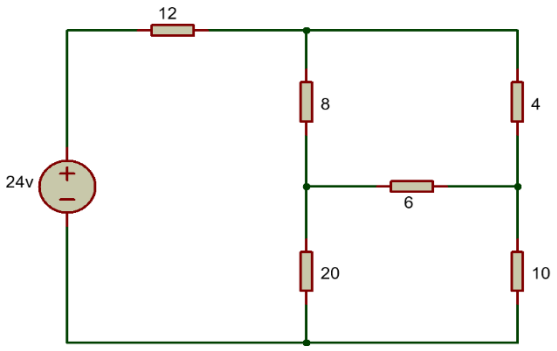5	Determine v_o and i in the circuit shown in Fig. 
6	Find currents and voltages in the circuit shown in Fig. 
7	Find the current loops i_1, and i_2 for the next circuit: 
8	Find the current loops i_1, i_2, and i_3 for the next circuit: 


9

: Find i_1 ,i_2 in the circuit :

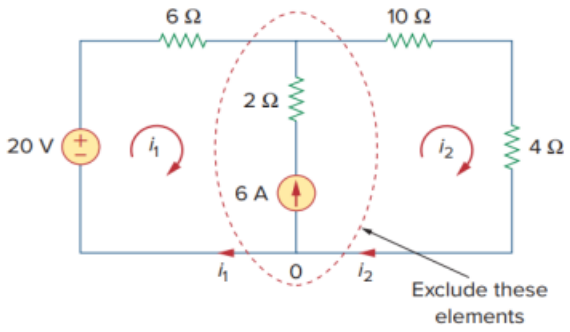


10

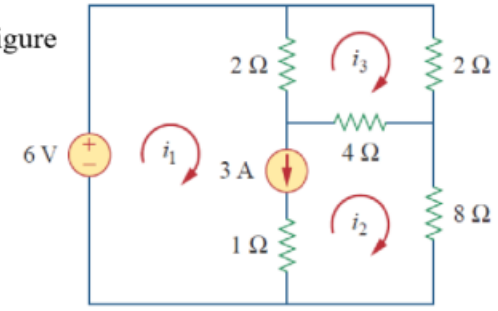Use mesh analysis to determine i_1, i_2, and i_3 in figure



11

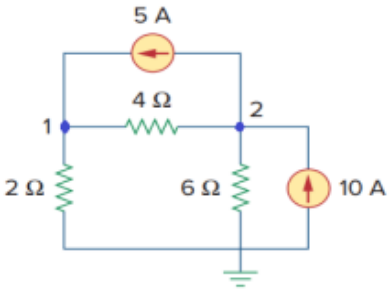Calculate the node voltages in the circuit shown in Fig.



12

Determine the voltages at the nodes in Fig.

