

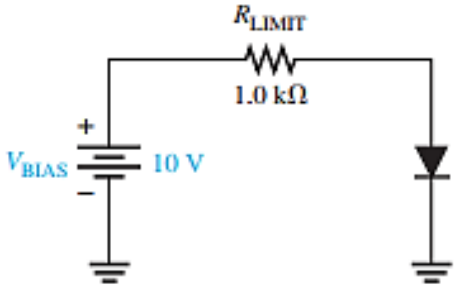
1 Determine the forward voltage and forward current for the diode in the figure below for each of the diode models. Also find the voltage across the limiting resistor in each case. Assume $r'_d = 10\ \Omega$ at the determined value of forward current.



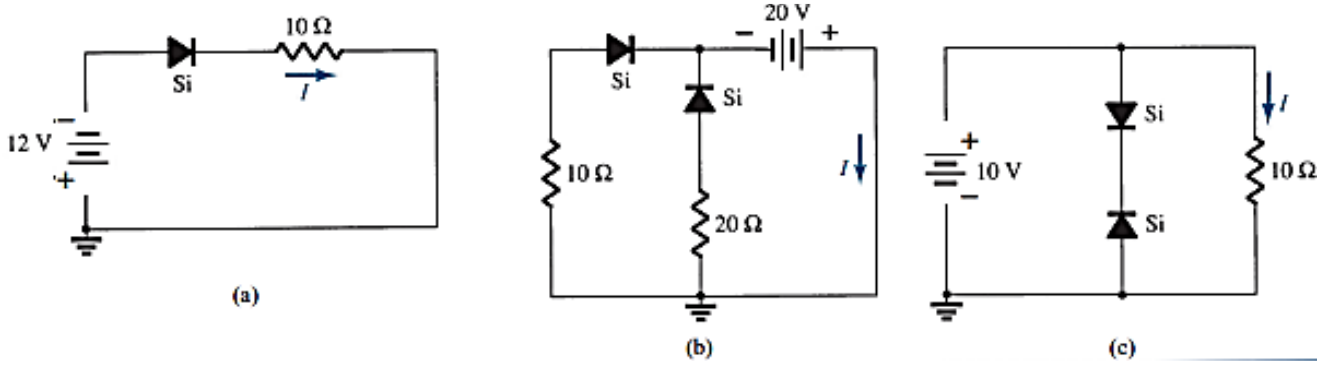
2 Determine the current I for each of the configurations using the approximate equivalent model for the diode.



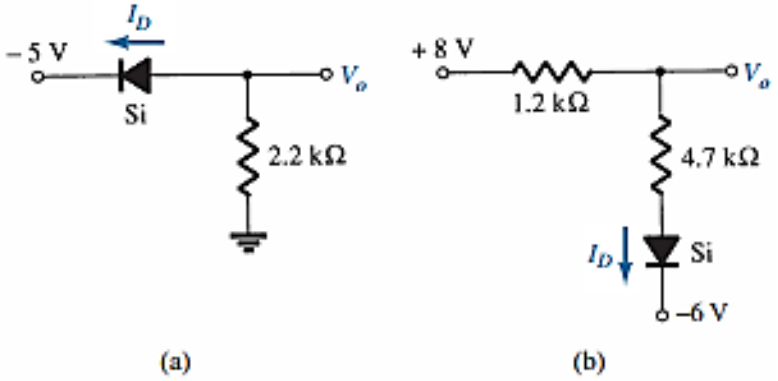
3 Determine V_o and I_D for the networks:




4 Determine the level of V_o

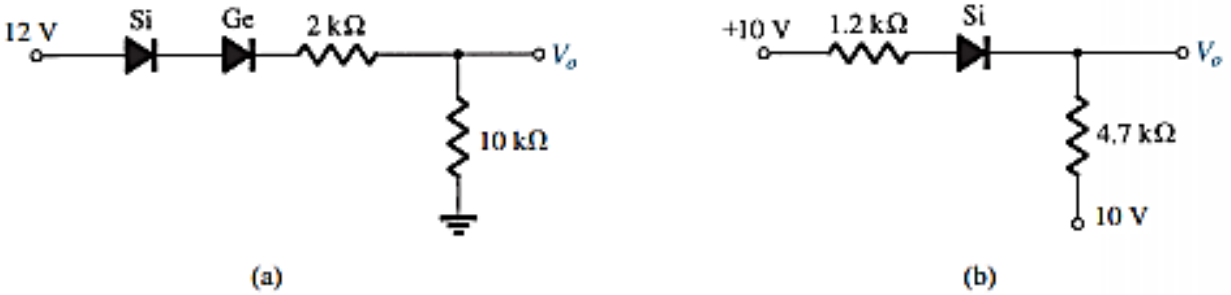

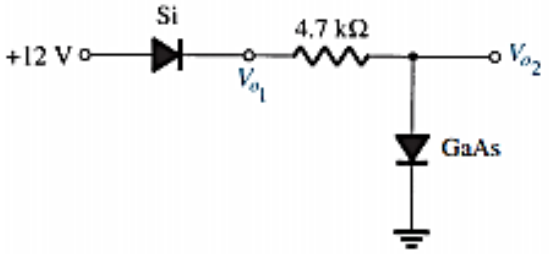5 Determine V_{o1} and V_{o2} for the networks:




(a)

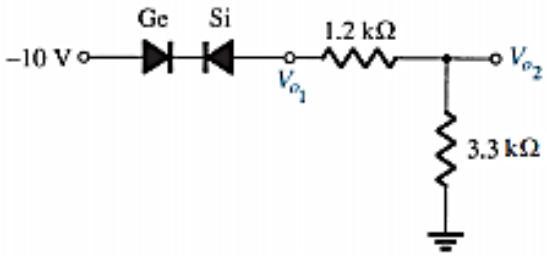


(b)

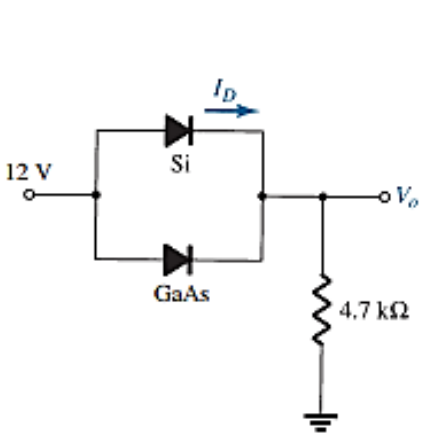6 Determine V_o and I_D for the networks:




(a)

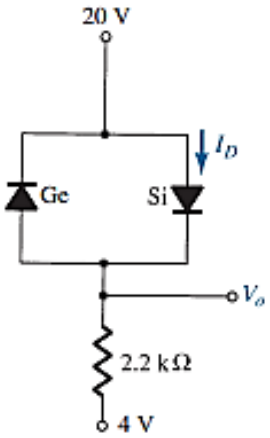


(b)

7 Determine V_o and I for the networks:

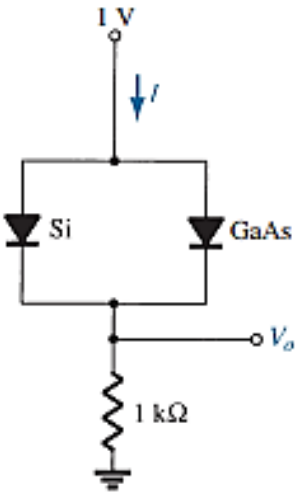


(a)

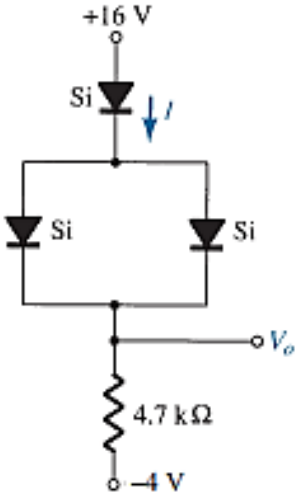


(b)

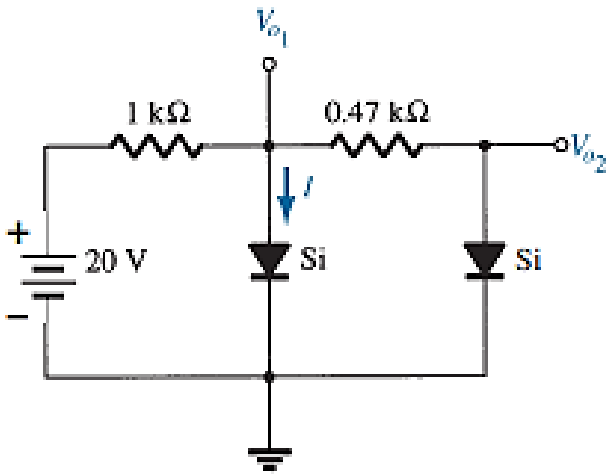8 Determine V_{o1} and V_{o2} for the network:



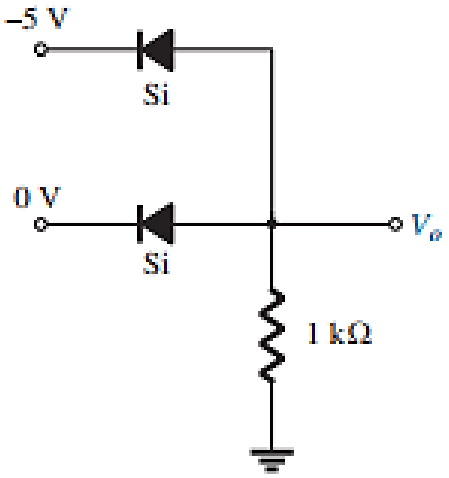9 Determine V_o for the negative logic OR gate:



10 Determine V_o for the negative logic AND gate:

