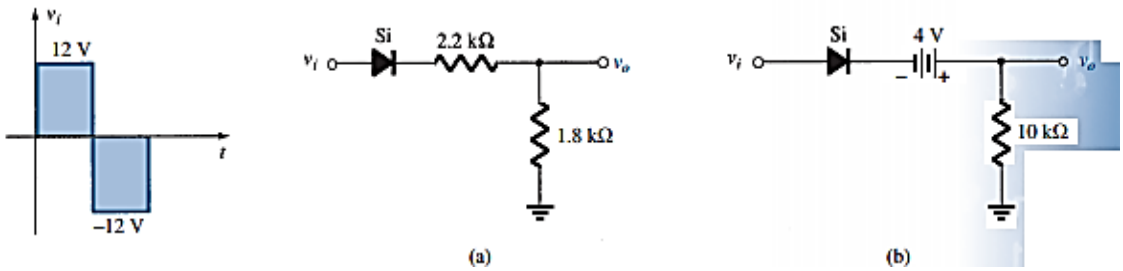
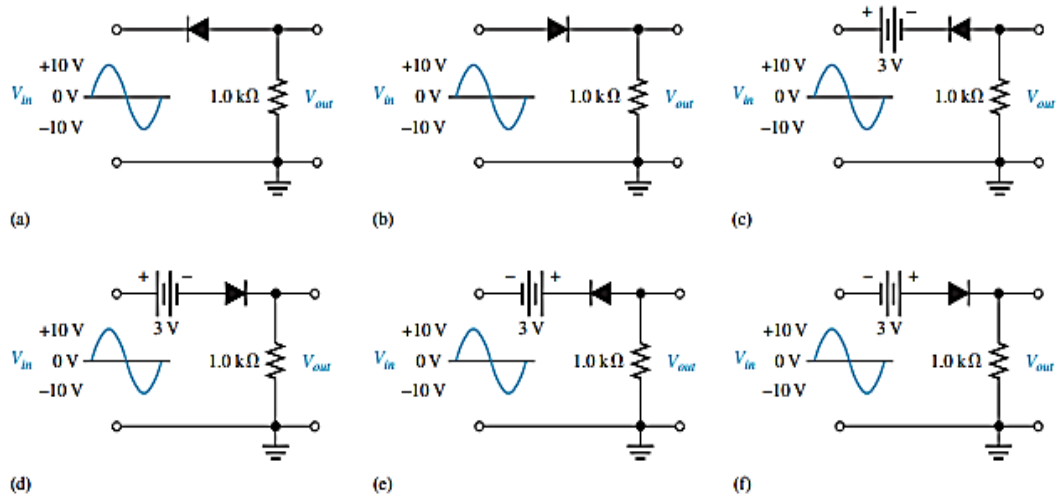
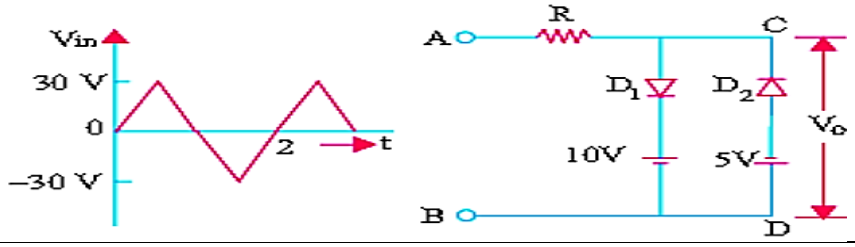
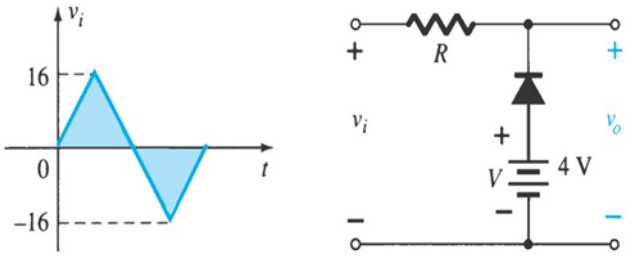
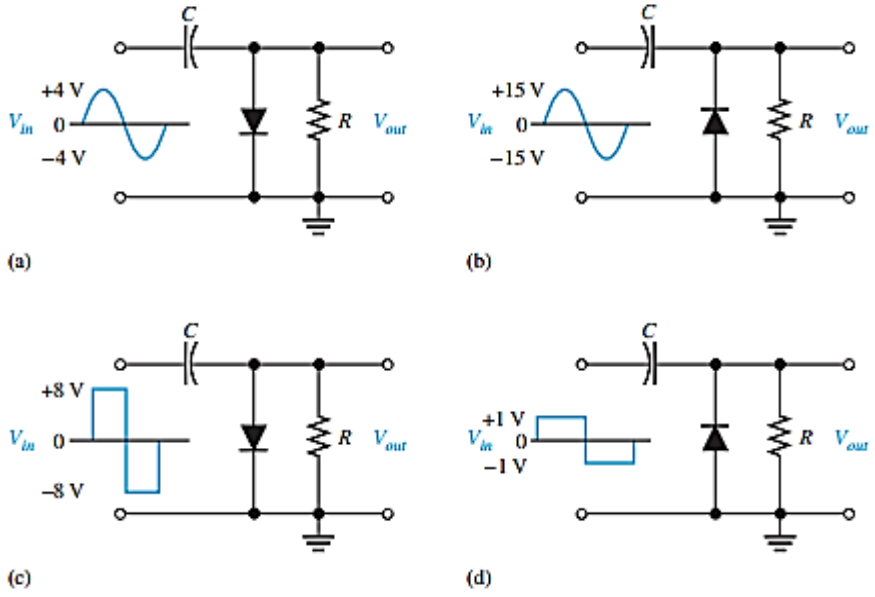
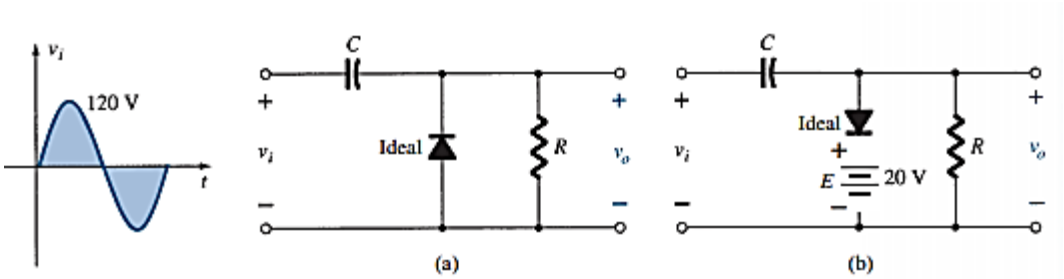
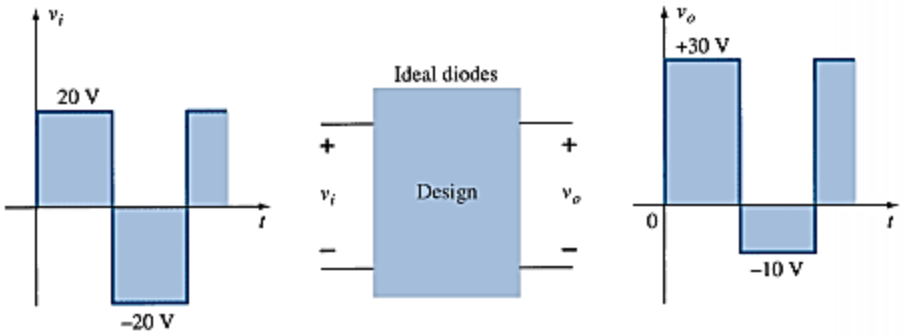
1	Determine Vo for each network: 
2	Determine the output voltage waveform for the following networks: 
3	Sketch the output (assume ideal diode) 
4	Sketch the output (assume practical diode) 

5	Describe the output waveform of each circuit below. Assume the RC time constant is much greater than the period of the input. 
6	Sketch vo for each network: 
7	Design a clamper to perform the indicated fuction below: 
8	A certain voltage doubler has 20 V rms on its input. What is the output voltage? Draw the circuit, indicating the output terminals and PIV rating for the diode. (b) Repeat Part(a) for a voltage Tripler and quadrupler